

# Electronics 4

## Third Year

Dr. Rania Fouad Ahmed

First Term

2023-2024

# References of Lecture Notes

- Prof. Dr. Soliman Mahmoud Lecture notes
- Prpf. Dr. Ahmed Nader Lecture Notes
- Prof. Dr. Razavi Lecture notes

# Administrative rules

## Course schedule

- Lecture : Sunday (2<sup>nd</sup> slot),
- Teaching assistant: Eng. Shymaa Emad

## Grading Policy

- Assignments and attendance: 10
- Quizzes: 10
- Mid term exam: 20,
- Oral exam:20
- Final exam: 90

# Course Outlines

date	subject
29/9/2024 (week 1)	Lecture 1 comparator circuits
13/10/2024 (week 3)	Lecture 2 analog multipliers
20/10/2024 (week 4)	Lecture 3 analog multipliers (Cont.)
27/10/2024 (week 5)	Lecture 4 opamp non-linear applications
3/11/2024 (week 6)	Lecture 5 voltage and current reference circuits
10/11/2024 (week 7)	Lecture 6 oscillators
17/11/2024 (week 8)	Midterm
24/11/2024 (week 9)	Lecture 7 oscillators (Cont.)
1/12/2024 (week 10)	Lecture 8 analog conditioning
8/12/2024 (week 11)	Lecture 9 CFOA active block
15/12/2024 (week 12)	Lecture 10 transconductance active block
22/12/2024 (week 13)	Lecture 11 review


# Text Book and References

- ***CMOS circuit design, layout and simulation, Fourth Edition by R. Jacob Baker***
- ***RF MICROELECTRONICS, Second Edition by Behzad Razavi***
- ***Design of Analog CMOS Integrated Circuits, second Edition, by Behzad Razavi***

# Nonlinear Analog Circuits

- *nonlinear analog circuits*: the inputs are not linearly related to the outputs.
- In particular, we discuss **voltage comparator** analysis and design, adaptive biasing
- and **analog multiplier** design.


# Basic CMOS Comparator Design

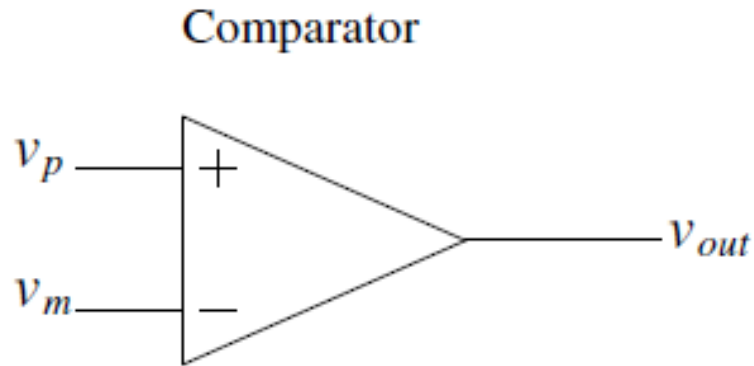

$v_p > v_m$  then  $v_{out} = VDD = \text{logic } 1$

$v_p < v_m$  then  $v_{out} = 0 = \text{logic } 0$


# Block diagram of a voltage comparator

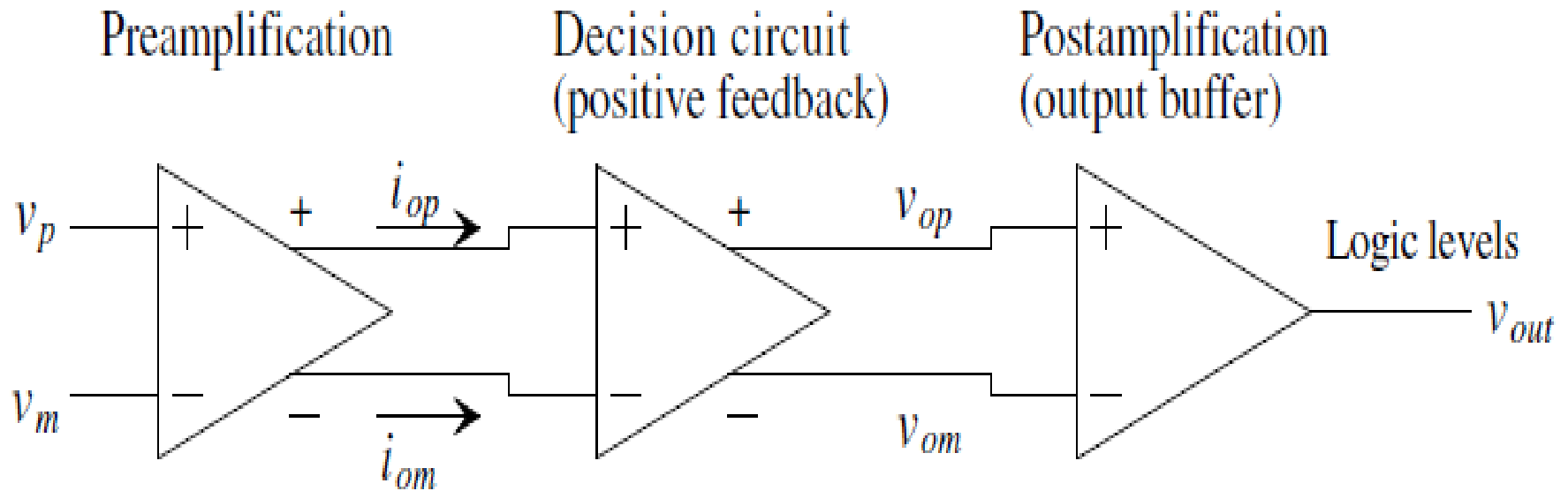



- The comparator consists of three stages: the input preamplifier, a positive feedback or decision stage, and an output buffer.
- The pre-amp stage: amplifies the input signal to improve the comparator sensitivity (i.e., increases the minimum input signal with which the comparator can make a decision) and isolates the input of the comparator from switching noise (often called kickback noise) coming from the positive feedback stage.
- The positive feedback stage: determines which of the input signals is larger.
- The output buffer: amplifies this information and outputs a digital signal.
- Designing a comparator can begin with considering input common-mode range, power dissipation, propagation delay, and comparator gain.

# Preamplification stage of comparator

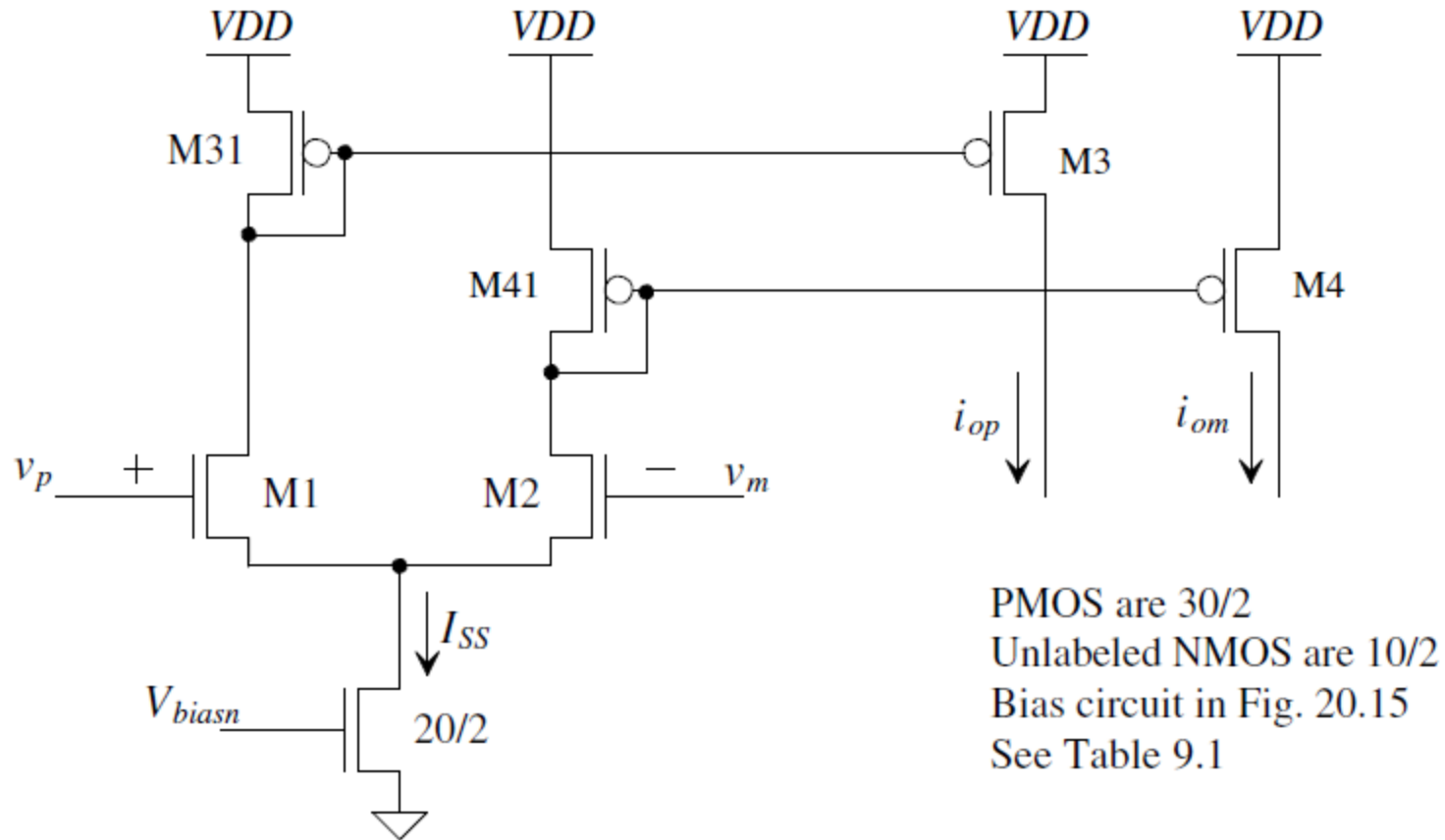


$$i_{op} = \frac{g_m}{2}(v_p - v_m) + \frac{I_{SS}}{2} = I_{SS} - i_{om}$$

# Positive feedback decision circuit

$$\beta_A = \beta_5 = \beta_8$$

$$\beta_B = \beta_6 = \beta_7$$

 

Let's begin by assuming that  $i_{op}$  is much larger than  $i_{om}$


M5 and M7 are on and M6 and M8 are off

$v_{om}$  is approximately 0 V

$$v_{op} = \sqrt{\frac{2i_{op}}{\beta_A}} + V_{THN}$$

$$\beta_A = \beta_5 = \beta_8$$

$$\beta_B = \beta_6 = \beta_7$$

 

When M8 is just about to turn on (M8's  $V_{GS}$  is approaching  $V_{THN}$  but the drain currents of M8 and M6 are still zero), the current flowing in M7 is

$$i_{om} = \frac{\beta_B}{2}(v_{op} - V_{THN})^2$$

and the current flowing in M5 is

$$i_{op} = \frac{\beta_A}{2}(v_{op} - V_{THN})^2$$


$$i_{op} = \frac{\beta_A}{\beta_B} \cdot i_{om}$$

If  $\beta_A = \beta_B$ , then switching takes place when the currents,  $i_{op}$  and  $i_{om}$ , are equal. Unequal  $\beta$ s cause the comparator to exhibit hysteresis. the switching point voltages:

$$V_{SPH} = v_p - v_m = \frac{I_{SS}}{g_m} \cdot \frac{\frac{\beta_B}{\beta_A} - 1}{\frac{\beta_B}{\beta_A} + 1} \text{ for } \beta_B \geq \beta_A$$
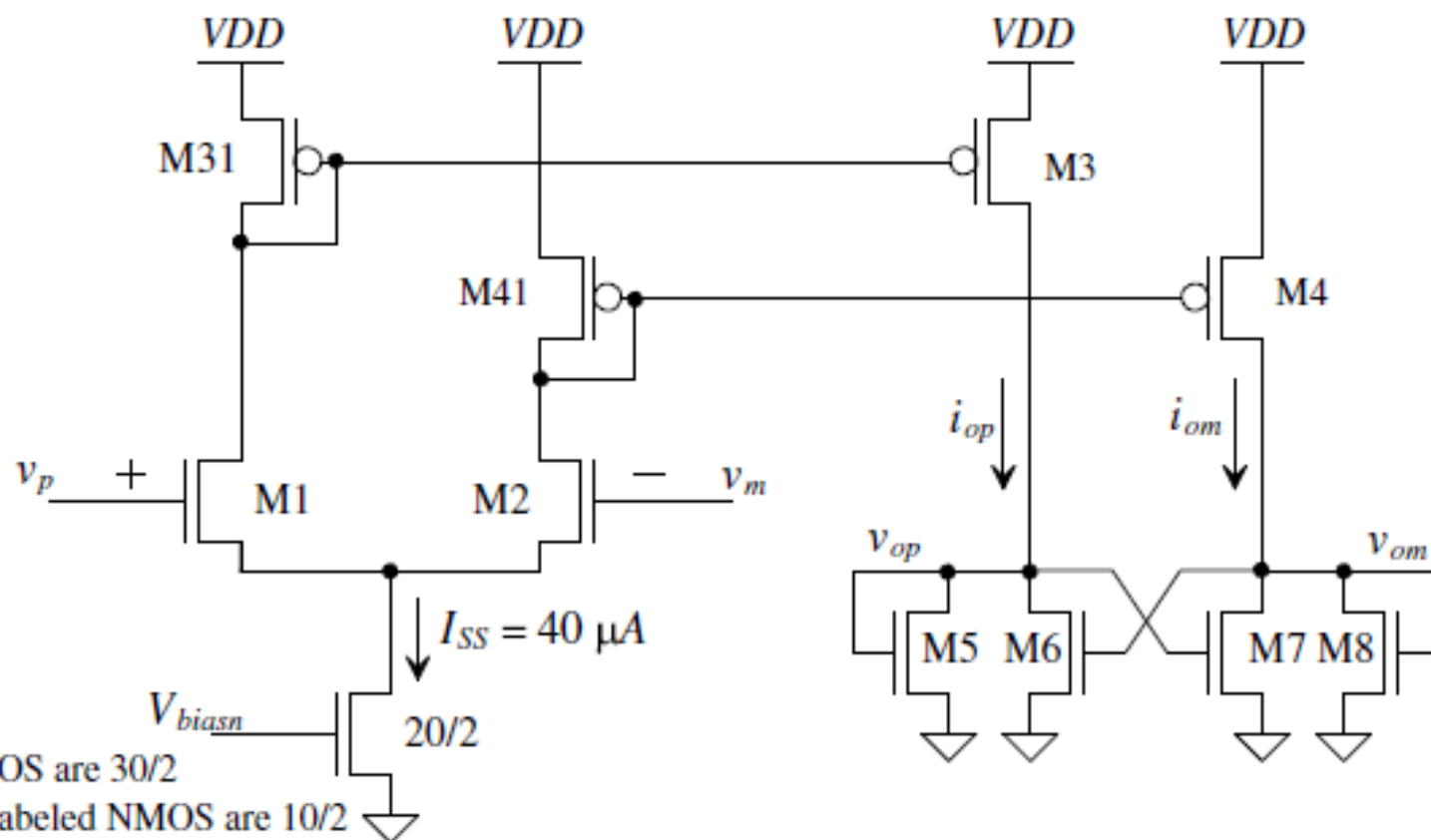
### Example 27.1

For the circuit shown in Fig. 27.5, estimate and simulate the switching point voltages for two designs: (1)  $W_5 = W_6 = W_7 = W_8 = 10$  with  $L = 1$  and (2)  $W_5 = W_8 = 10$  and  $W_6 = W_7 = 12$  with  $L = 1$ .



PMOS are 30/2


Unlabeled NMOS are 10/2

Bias circuit in Fig. 20.15


See Table 9.1

$$\beta_A = \beta_B = 120 \frac{\mu A}{V^2} \cdot \frac{10}{1} = 1.2 \text{ mA/V}^2$$

$$V_{SPH} = V_{SPL} = 0.$$

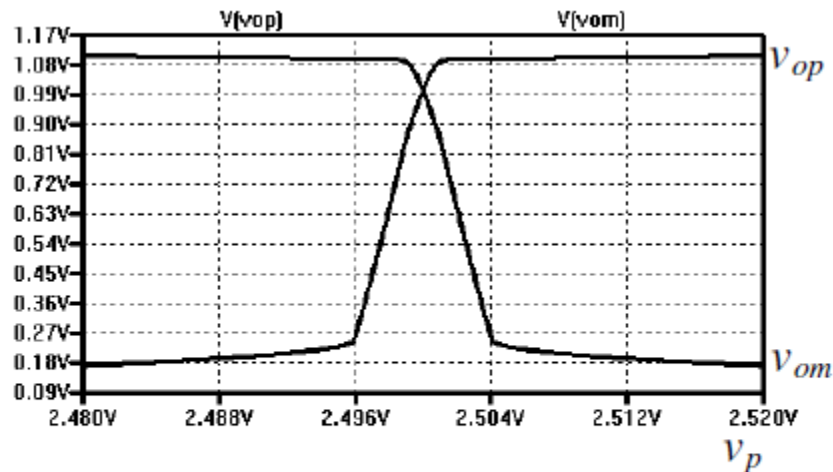

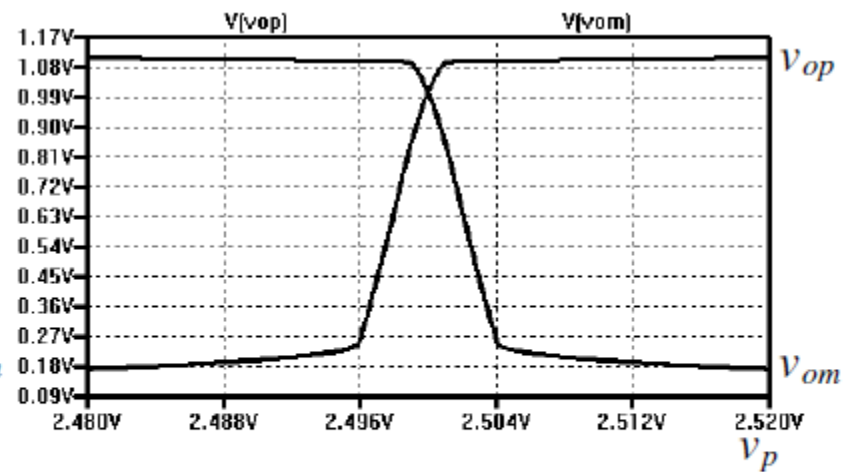(a) Minus input held at 2.5 V while the positive input is swept from 2.48 to 2.52 V.




(b) Minus input held at 2.5 V while the positive input is swept from 2.52 to 2.48.

For the second case

$$\beta_A = 120 \frac{\mu\text{A}}{\text{V}^2} \cdot \frac{10}{1} \quad \text{and} \quad \beta_B = 120 \frac{\mu\text{A}}{\text{V}^2} \cdot \frac{12}{1}$$

with  $I_{SS} = 40 \mu\text{A}$  and  $g_m = 150 \mu\text{A/V}$
 
$$V_{SPH} = -V_{SPL} = \frac{I_{SS}}{g_m} \cdot \frac{\frac{\beta_B}{\beta_A} - 1}{\frac{\beta_B}{\beta_A} + 1} = \frac{40}{150} \cdot \frac{1.2 - 1}{1.2 + 1} = 24 \text{ mV}$$






# *Output Buffer*

- The main purpose of the output buffer is to convert the output of the decision circuit into a logic signal (i.e., 0 or *VDD*).
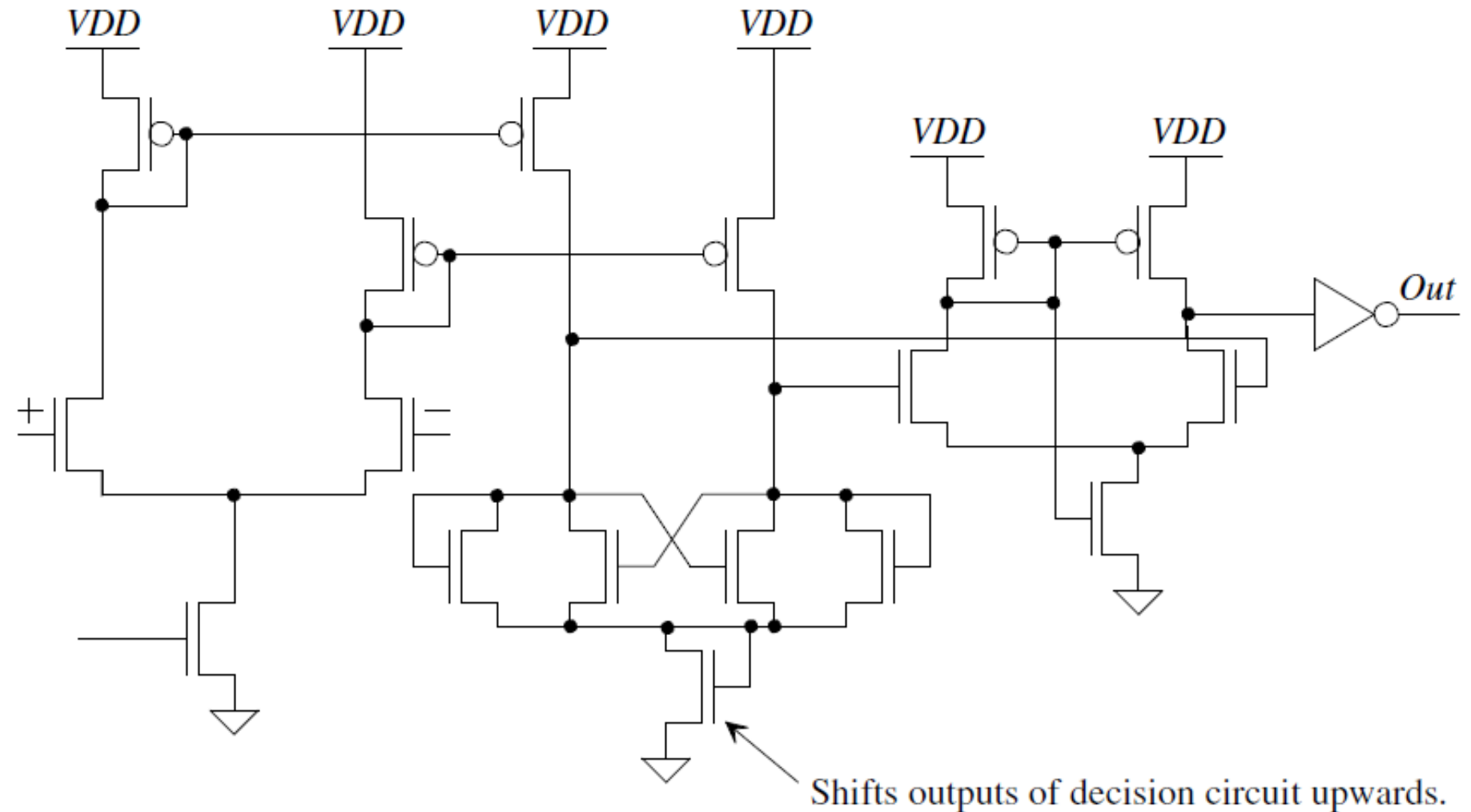
# Using a self-biased diff-amp for the output buffer



*End of Lecture 1*