

Electronics5

Lecture 1

Dr. Rania Fouad Ahmed

Administrative rules

- Lecture : Sunday (4st slot), 1:00-3:00
- Teaching assistant: Eng. Shymaa Emad
- Grading Policy
 - Assignments: 5
 - Quizzes: 10
 - Mid term exam: 20
 - Oral exam: 15
 - Final exam: 75

Course schedule


date	subject
29/9/2024 (week 1)	Lecture 1 introduction to VLSI
13/10/2024 (week 3)	Lecture 2 inverter switching characteristics
20/10/2024 (week 4)	Lecture 3 combinational logic circuits
27/10/2024 (week 5)	Lecture 4 delay
3/11/2024 (week 6)	Lecture 5 delay (Cont.)
10/11/2024 (week 7)	Lecture 6 power
17/11/2024 (week 8)	Midterm
24/11/2024 (week 9)	Lecture 7 interconnects
1/12/2024 (week 10)	Lecture 8 interconnects (Cont.)
8/12/2024 (week 11)	Lecture 9 Sequential circuits
15/12/2024 (week 12)	Lecture 10 Dynamic circuits
22/12/2024 (week 13)	Lecture 11 review

Outline


- Operation of MOS Transistors
- CMOS circuits
- CMOS Gate Design
- Pass Transistors
- Transmission Gates

MOS Transistors

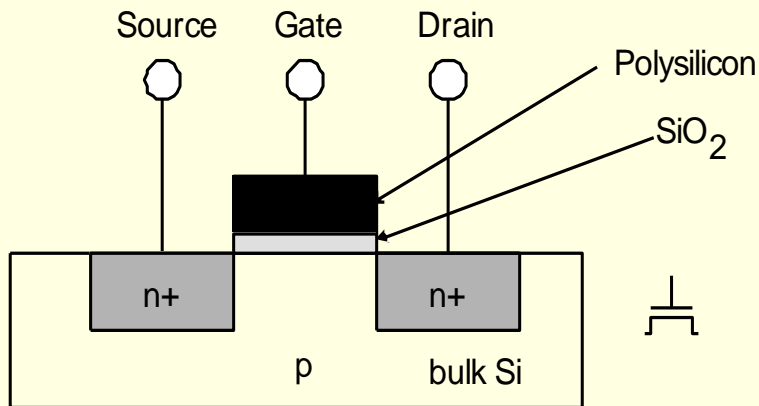- Four terminal device: gate, source, drain, body
- Gate – oxide – body stack looks like a capacitor
 - Gate and body are conductors (body is also called the substrate)
 - SiO_2 (oxide) is a “good” insulator (separates the gate from the body)
 - Called metal–oxide–semiconductor (MOS) capacitor, even though gate is mostly made of poly-crystalline silicon (polysilicon)




NMOS

 

PMOS


NMOS Operation

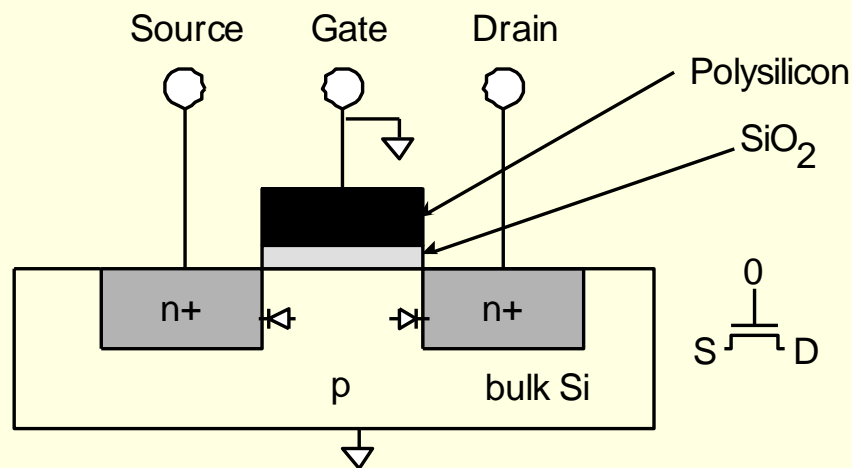- Body is commonly tied to ground (0 V)
- Drain is at a higher voltage than Source
- When the gate is at a low voltage:
 - P-type body is at low voltage
 - Source-body and drain-body “diodes” are OFF
 - No current flows, transistor is OFF




NMOS Operation Cont.

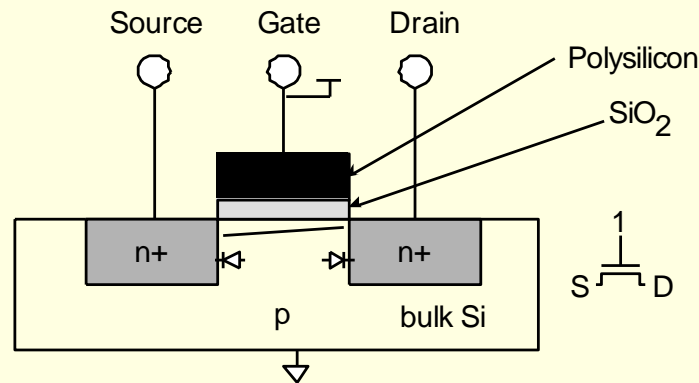- When the gate is at a high voltage: Positive charge on gate of MOS capacitor
 - Negative charge is attracted to body under the gate
 - Inverts a channel under gate to “n-type” (N-channel, hence called the NMOS) if the gate voltage is above a threshold voltage (V_T)
 - Now current can flow through “n-type” silicon from source through channel to drain, transistor is ON



PMOS Transistor

 - Similar, but doping and voltages reversed
 - Body tied to high voltage (V_{DD})
 - Drain is at a lower voltage than the Source
 - Gate low: transistor ON
 - Gate high: transistor OFF
 - Bubble indicates inverted behavior




Power Supply Voltage

- $GND = 0\text{ V}$
- In 1980's, $V_{DD} = 5\text{V}$
- V_{DD} has decreased in modern processes
 - High V_{DD} would damage modern tiny transistors
 - Lower V_{DD} saves power
- $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0,$



Transistors as Switches

 - In Digital circuits, MOS transistors are electrically controlled switches
- Voltage at gate controls path from source to drain





CMOS Inverter

A	Y
0	
1	

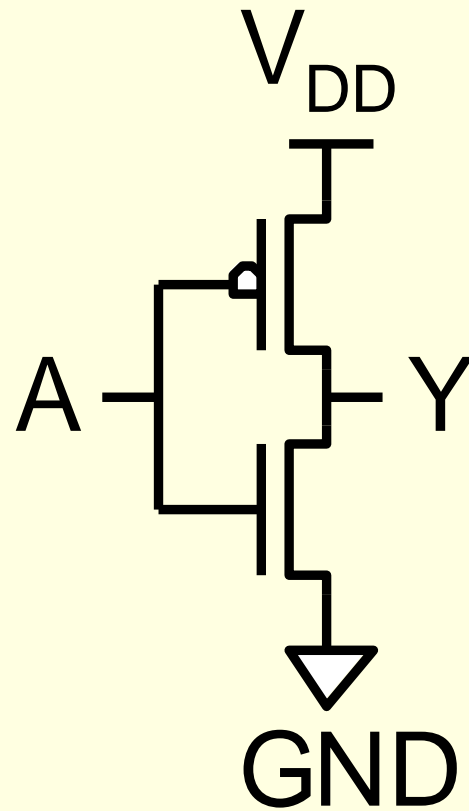 

CMOS Inverter



A	Y
0	
1	0

  

Y is pulled low by the turned on NMOS Device. Hence NMOS is the pull-down device.

CMOS Inverter



A	Y
0	1
1	0

  

Y is pulled high by the turned on PMOS Device. Hence PMOS is the pull-up device.



CMOS NAND Gate

A	B	Y
0	0	
0	1	
1	0	
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	
1	0	
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

  


CMOS NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

  


3-input NAND Gate

 - Y is pulled low if ALL inputs are 1
- Y is pulled high if ANY input is 0




CMOS Gate Design

- A 4-input CMOS NOR gate

 

Complementary CMOS

 
- Complementary CMOS logic gates
 - nMOS *pull-down network*
 - pMOS *pull-up network*
 - a.k.a. static CMOS



	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)

Series and Parallel

 - nMOS: 1 = ON
- pMOS: 0 = ON
- *Series*: both must be ON
- *Parallel*: either can be ON




Conduction Complement

- Complementary CMOS gates always produce 0 or 1

- Ex: NAND gate

 - Series nMOS: $Y=0$ when both inputs are 1
- Thus $Y=1$ when either input is 0
- Requires parallel pMOS



- Rule of *Conduction Complements*





- Pull-up network is **complement** of pull-down
- Parallel \rightarrow series, series \rightarrow parallel

Compound Gates

- *Compound gates* can do any inverting function

- Ex: AND-AND-OR-INV (AOI22)
    
$$Y = \overline{(A \bullet B) + (C \bullet D)}$$




Example: O3AI

- $Y = \overline{(A + B + C)} \bullet D$



Example: O3AI

■
$$Y = \overline{(A + B + C)} \cdot D$$

 











Pass Transistors

- Transistors can be used as switches

  

Pass Transistors

- Transistors can be used as switches

          

Signal Strength


- *Strength* of signal
 - How close it approximates ideal voltage source
- V_{DD} and GND rails are strongest 1 and 0
- nMOS pass strong 0
 - But degraded or weak 1
- pMOS pass strong 1
 - But degraded or weak 0
- Thus NMOS are best for pull-down network
- Thus PMOS are best for pull-up network


Transmission Gates


- Pass transistors produce degraded outputs
- *Transmission gates* pass both 0 and 1 well

Transmission Gates

 - Pass transistors produce degraded outputs
- *Transmission gates* pass both 0 and 1 well



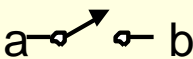$g = 0, gb = 1$

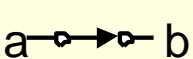
 
 
 
$g = 1, gb = 0$


Input

Output

$g = 1, gb = 0$
 0 → strong 0

$g = 1, gb = 0$
 1 → strong 1



END OF LECTURE 1